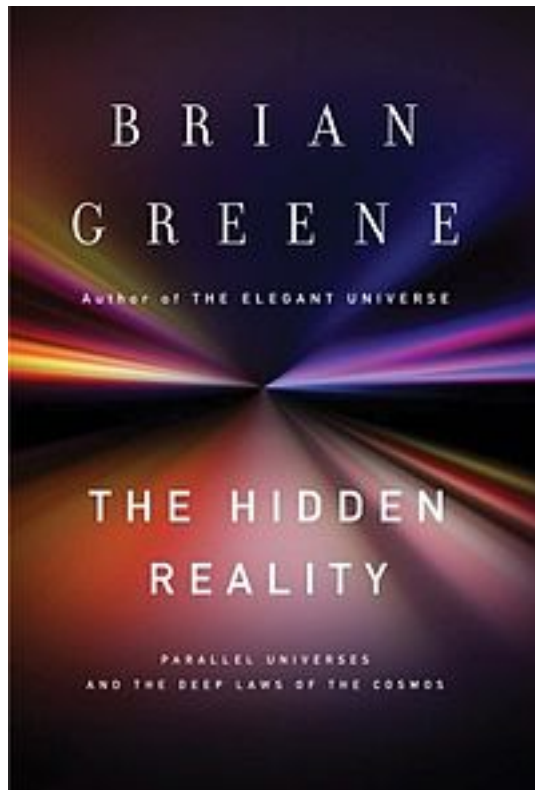


Chapter 20

Capacitors, Resistors and Batteries

Brian Greene, Nov 6 @ 7pm

Elliott Hall of Music



Free seating pass required for entry

<http://www.convocations.org/portfolio/brian-greene-11-6-14/#sthash.KqvAENA9.dpuf>

Announcements

EXAM II is Tuesday

8-10 PM – TUESDAY, Nov. 4 in Elliot Hall of Music

Material: Chapters 17, 18, and 19 in the book.

How to Study:

Practice Exam + Solutions + Eqn Sheet is on BBL.

(Note the practice exam has some
Ch 20 material, but your exam will not)

Find the WebAssign Extended Practice Problems

- not for credit, but you get 50 tries for ALL questions in Ch 17-19

Last Time




- Solving for $Q(t)$ and $I(t)$ in an RC circuit
- The "time constant" of an RC circuit is RC

RC Circuit: Summary

$$Q = CV$$




$$V = IR$$

$$I = \frac{dQ}{dt}$$

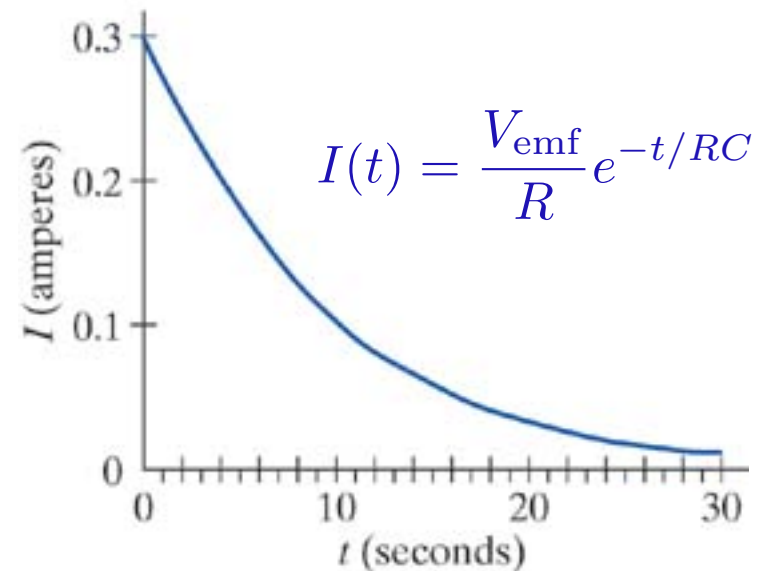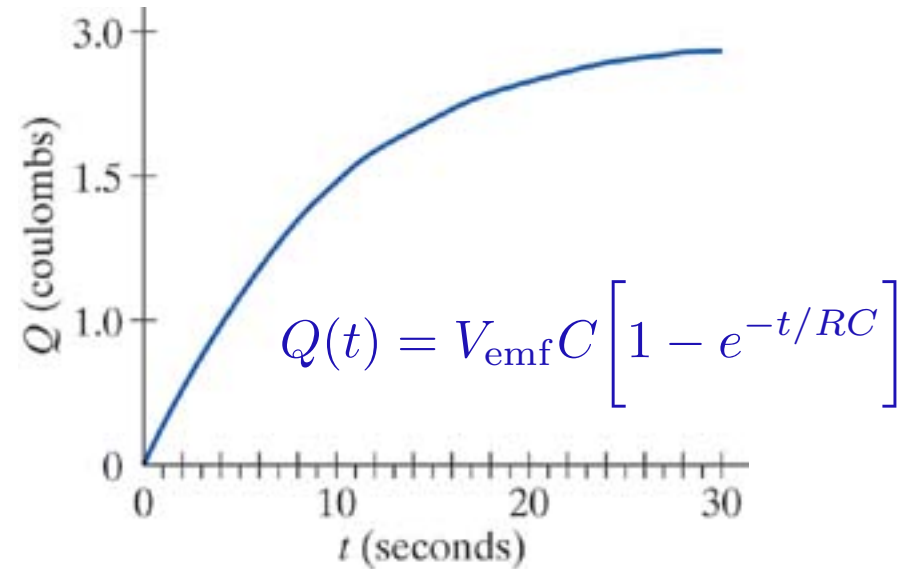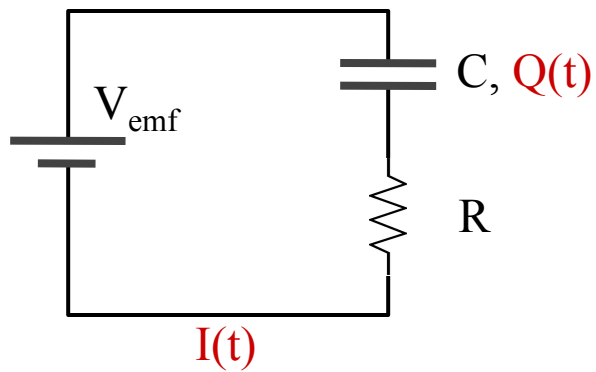




Clicker Q. 1

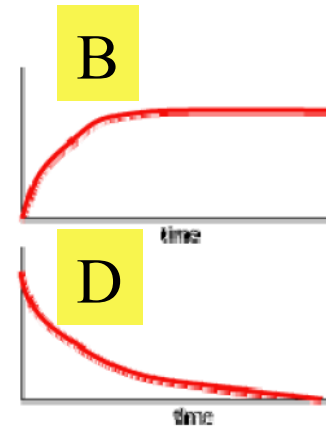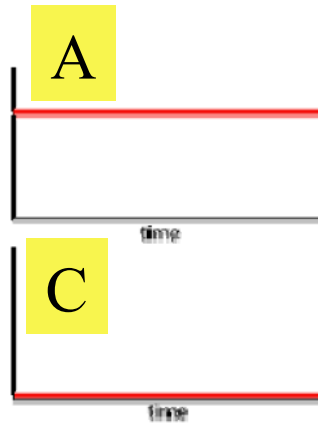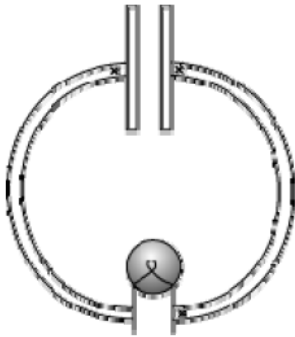Capacitor initially charged. Which graph shows CURRENT vs TIME while DISCHARGING?




Clicker Q. 1

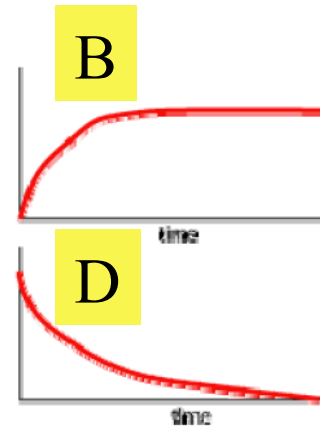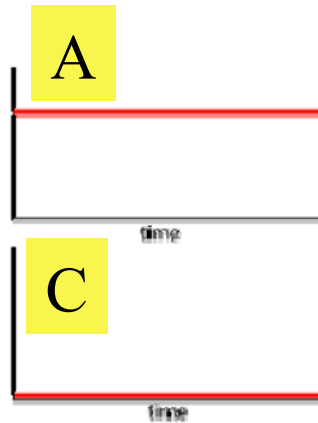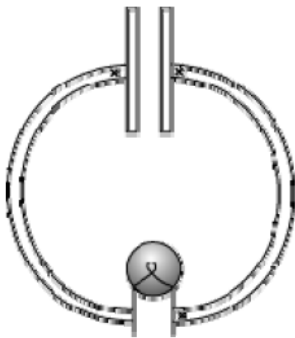Capacitor initially charged. Which graph shows CURRENT vs TIME while DISCHARGING?




D

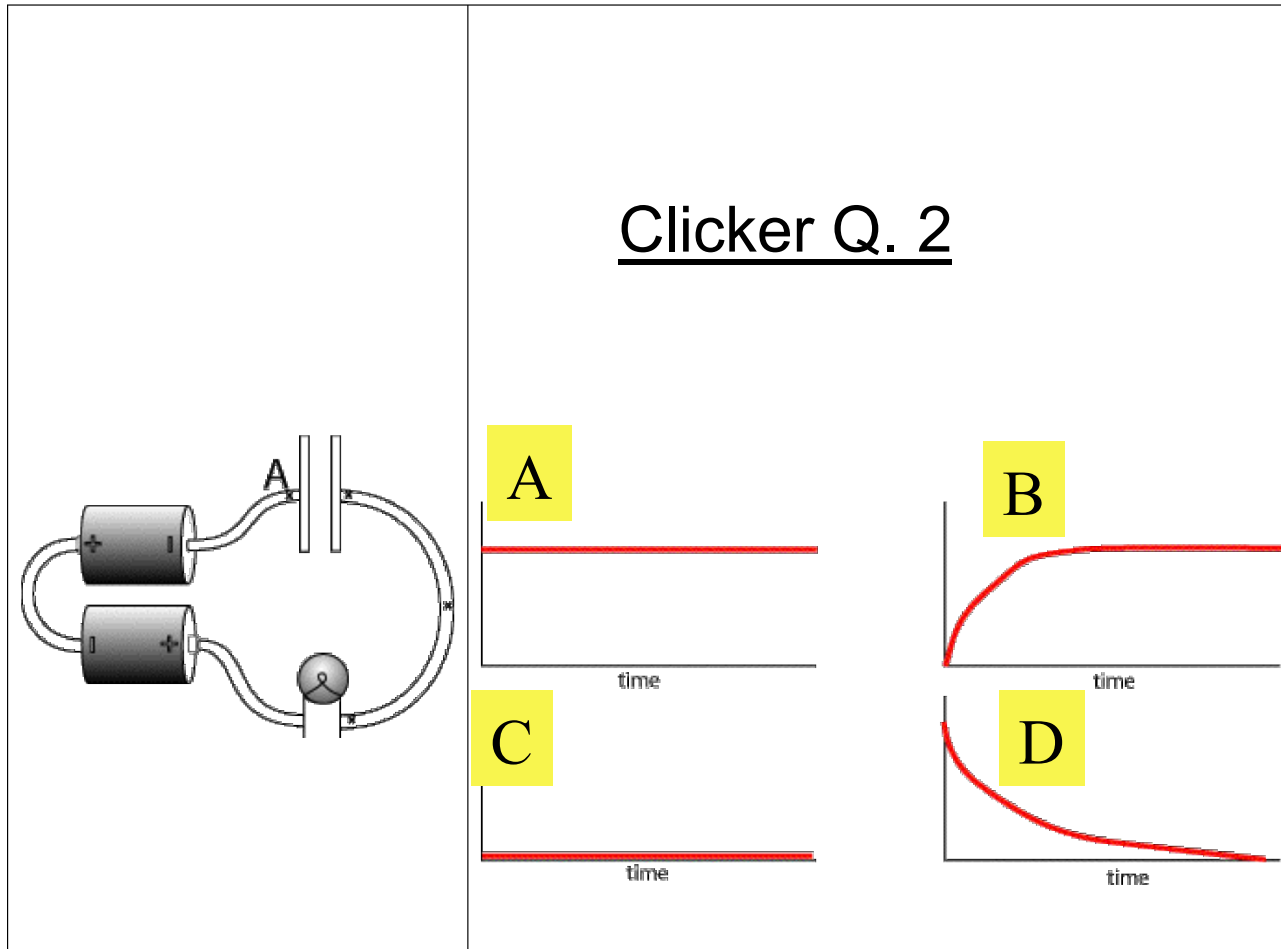Capacitor initially uncharged. Which graph shows the magnitude of the POTENTIAL DIFFERENCE across the LIGHT BULB FILAMENT while CHARGING?



Capacitor initially uncharged. Which graph shows the magnitude of the POTENTIAL DIFFERENCE across the LIGHT BULB FILAMENT while CHARGING?



D

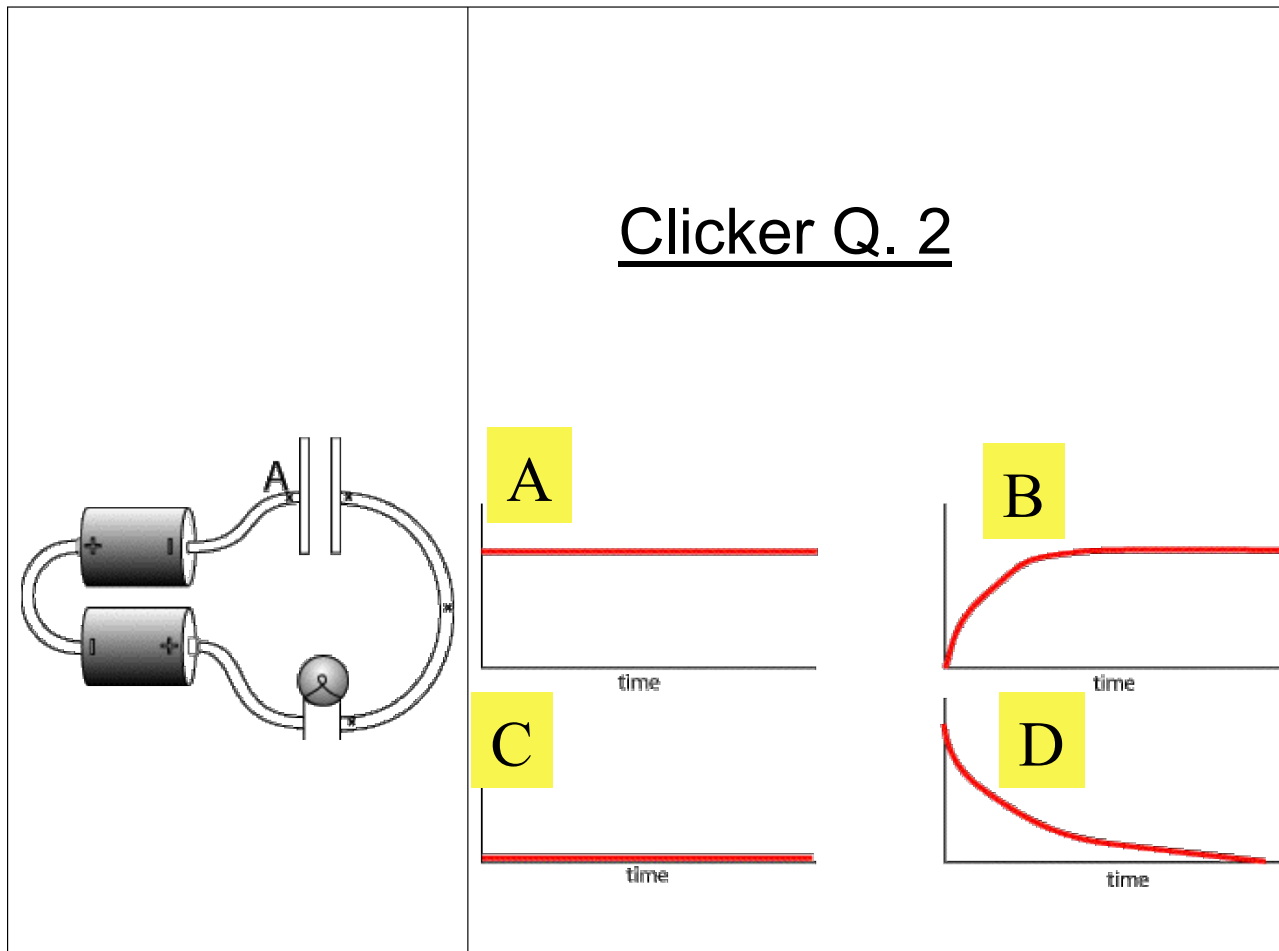

Today

- Ohm's Law
- Series and Parallel Resistors
- Series and Parallel Capacitors
- Ammeters, Voltmeters, Ohmmeters, Oh my!

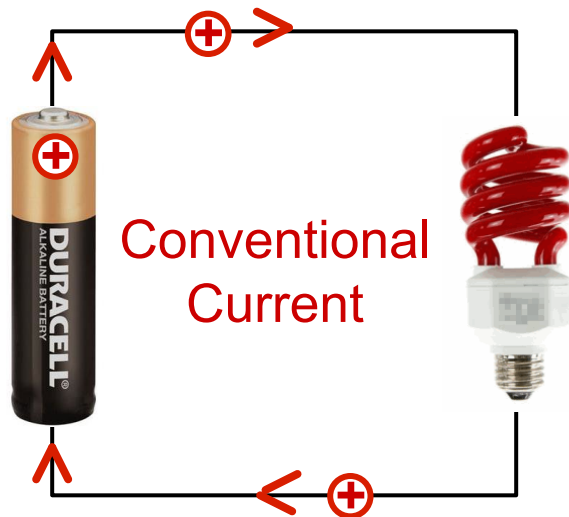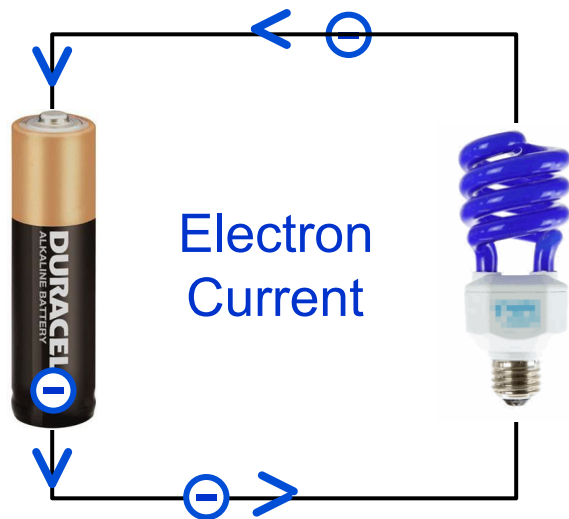Conventional Current and Electron Current



Electron Current:

$$i = nA\bar{v} = \left[\frac{\text{electrons}}{\text{second}} \right]$$

Square Brackets []
Mean "Units"

Conventional Current:

$$I = |q|nA\bar{v} = \left[\frac{\text{Coulombs}}{\text{second}} \right] \\ = \left[\text{Amperes} \right]$$


Blast from the Past:
Lecture 12

Current Density & Conductivity

$$I = |q|nA\bar{v}$$

$$\bar{v} = u\bar{E}$$

$$\vec{J} = \sigma \vec{E}$$

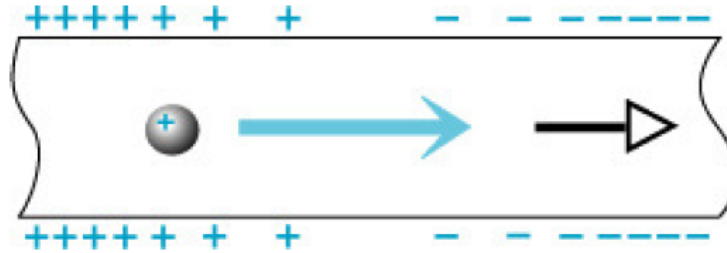

The conductivity is a material-dependent quantity:

The current density has magnitude $J = I / A$


$$\sigma = |q|n u$$

carrier density

carrier charge

mobility

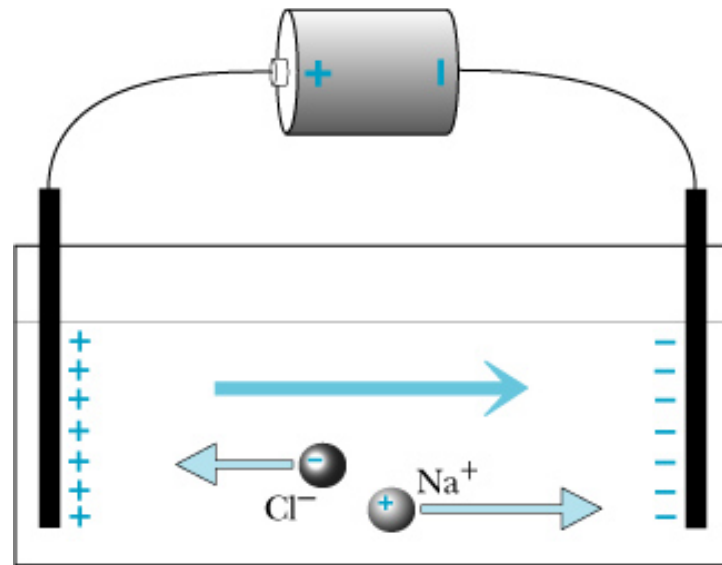
Conductivity with two kinds of charge carrier



$$\sigma = |q_1|n_1u_1 + |q_2|n_2u_2$$

Definition of Resistance

$$R = \frac{L}{\sigma A}$$

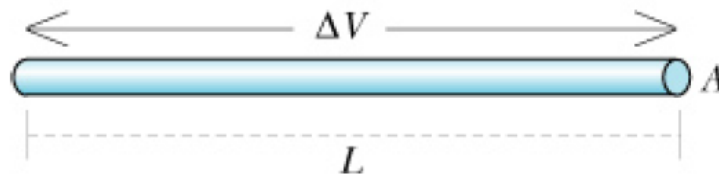

Important special case: if the conductivity remains constant regardless of how much current flows, then we call the material “ohmic” and any piece of the material obeys “Ohm’s Law”:

$$I = \text{constant} \times |\Delta V|$$

Non-ohmic examples: diodes, capacitors, batteries.

“Ohmic” Resistors

$$|\Delta V| = I R$$

$$R = \frac{L}{|q| n A u} \quad \text{depends on both material properties and geometry}$$

Never write $V = I R$ because ...

... what you really mean is $|\Delta V| = I R$

Series and Parallel

Series: One right after the other.
(Same current through each)

Parallel: Elements are “next to” each other.
(Same voltage across each)

Series Resistance


$$\Delta V_{\text{batt}} + \Delta V_1 + \Delta V_2 + \Delta V_3 = 0$$

$$emf - R_1 I - R_2 I - R_3 I = 0$$

$$emf = R_1 I + R_2 I + R_3 I$$

$$emf = (R_1 + R_2 + R_3) I$$

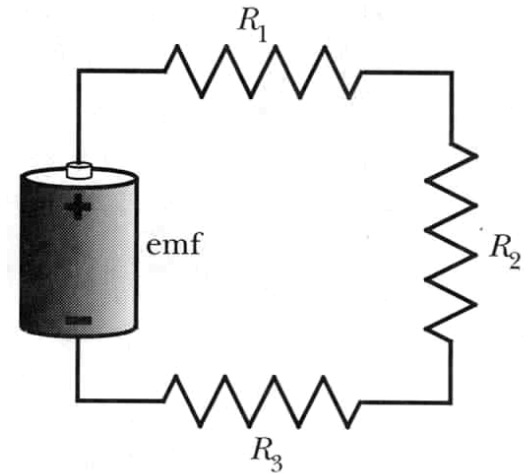
$$emf = R_{\text{equivalent}} I, \text{ where } R_{\text{equivalent}} = R_1 + R_2 + R_3$$



For resistors made of the same material and with the same A it follows straight from the definition of resistance:

$$R = \frac{L}{\sigma A}$$

Parallel Resistance

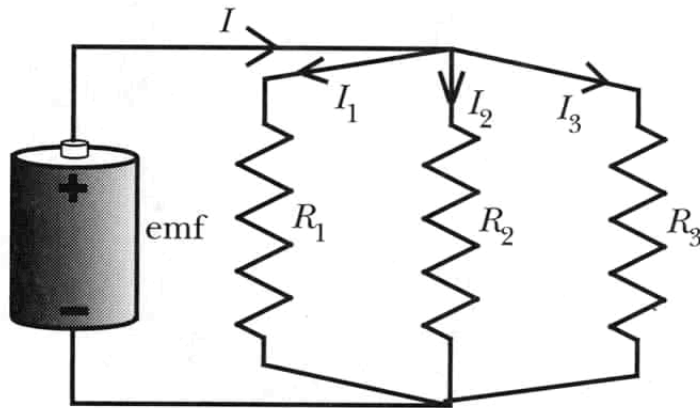

$$I = I_1 + I_2 + I_3$$

$$I = \frac{emf}{R_1} + \frac{emf}{R_2} + \frac{emf}{R_3}$$

$$I = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) emf = \frac{emf}{R_{equivalent}}$$

$$\frac{1}{R_{equivalent}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


For resistors made of the same material and with the same A it follows straight from the definition of resistance:

$$R = \frac{L}{\sigma A} \longrightarrow \frac{1}{R} = \frac{\sigma A}{L}$$

$$A_{equivalent} = A_1 + A_2 + A_3$$


Parallel Capacitors

$$C = \frac{\epsilon_0 A}{s}$$

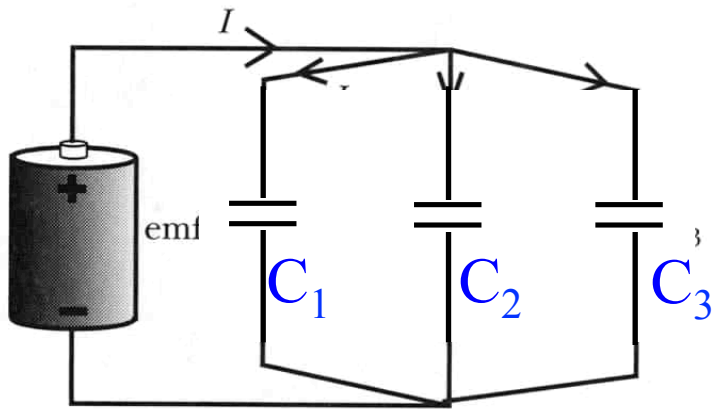

$$C_{\text{eff}} = C_1 + C_2 + C_3$$


Equivalent to:

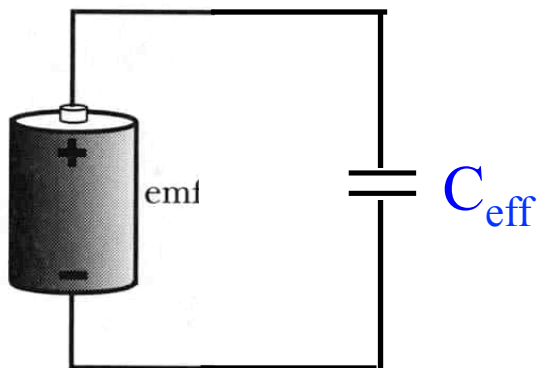

Parallel Capacitors ADD


Series Capacitors

$$C = \frac{\epsilon_0 A}{s}$$

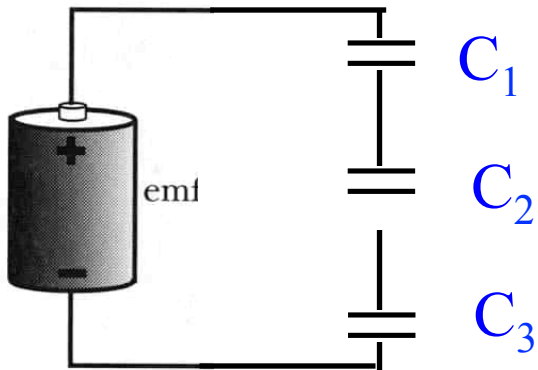

$$\frac{1}{C_{\text{eff}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

Equivalent to:

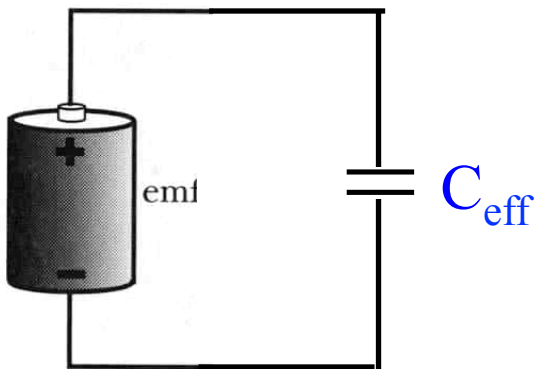

Resistors and Capacitors

Resistors in Series

$$R_{\text{eff}} = R_1 + R_2 \quad \text{ADD}$$

Capacitors in Parallel

$$C_{\text{eff}} = C_1 + C_2$$

Resistors in Parallel

$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Capacitors in Series

$$\frac{1}{C_{\text{eff}}} = \frac{1}{C_1} + \frac{1}{C_2}$$

iClicker Question

time constant = RC

Ammeters, Voltmeters and Ohmmeters


Ammeter: measures current I (*Amps*)

Voltmeter: measures voltage difference ΔV (*Volts*)

Ohmmeter: measures resistance R (*Ohms*)

Ammeter Design: r_{int}

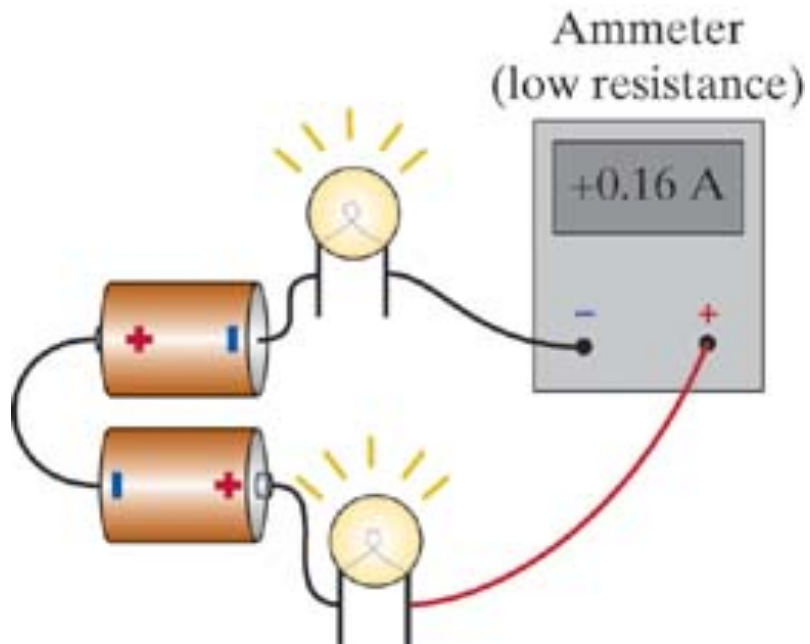
Ammeter is inserted in series into a circuit – measured current flows through it.



You have to get in the flow to measure the current.

Ammeter Design: r_{int}

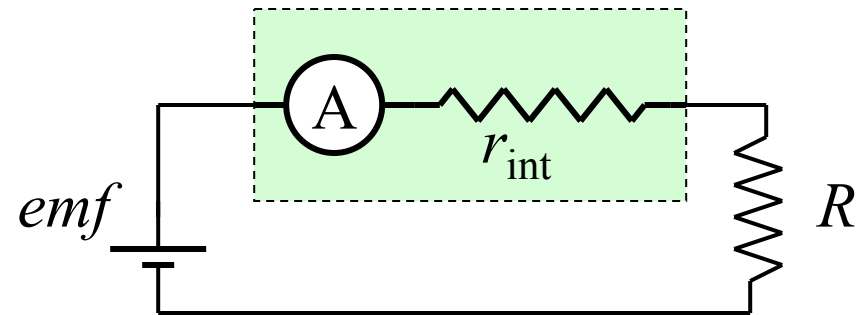Ammeter is inserted in series into a circuit – measured current flows through it.




No ammeter: $emf - RI = 0 \longrightarrow I = \frac{emf}{R}$

With ammeter: $emf - r_{\text{int}}I - RI = 0 \longrightarrow I = \frac{emf}{R + r_{\text{int}}}$

Internal resistance of an ammeter must be very small

Voltmeter

Voltmeters measure potential difference

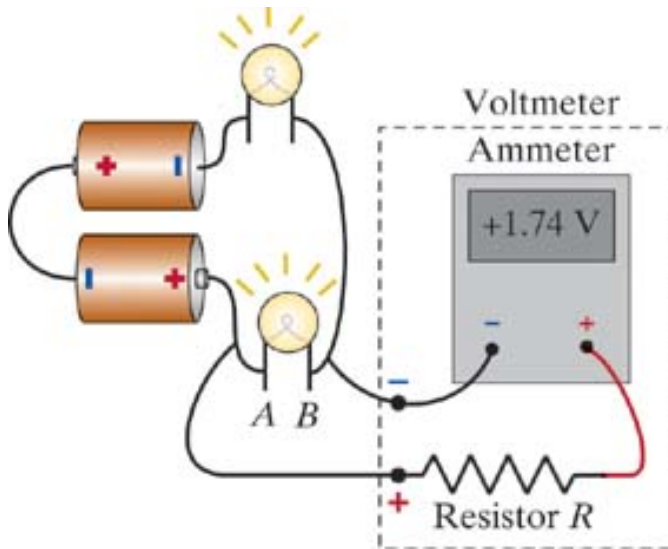

ΔV_{AB} – add a series resistor to ammeter

$$I = \frac{\Delta V}{R}$$

Measure I and convert to $\Delta V_{AB} = IR$


Voltmeter needs
high internal resistance.

Connecting Voltmeter:

Higher potential must be connected to the '+' socket and lower one to the '-' socket to result in positive reading.

Ohmmeter

How would you measure R?

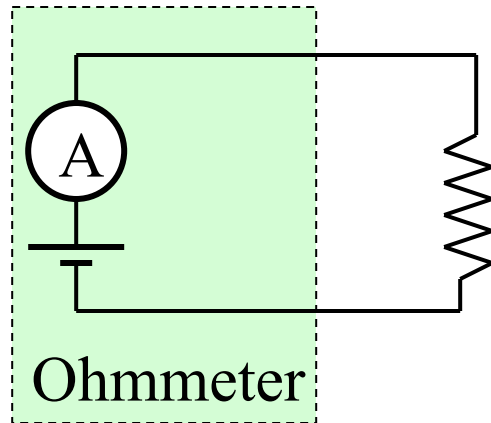

$$R = \frac{emf}{I}$$

$$I = \frac{emf}{R}$$

Ammeter with a small voltage source

Today

- Ohm's Law
- Series and Parallel Resistors
- Series and Parallel Capacitors
- Ammeters, Voltmeters, Ohmmeters, Oh my!